

Reference for Homework 2

Wu Daiyang


August 26, 2024

Please read the preface before reading this document!!!

1

In a three-capacitor, $C_1 = 10.0\mu\text{F}$, $C_2 = 20.0\mu\text{F}$, and $C_3 = 25.0\mu\text{F}$. If no capacitor can withstand a potential difference of more than 100 V without failure, what are

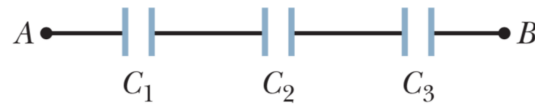- (a) the magnitude of the maximum potential difference that can exist between points A and B and
- (b) the maximum energy that can be stored in the three-capacitor arrangement?



Reference:

$$(a) \Rightarrow Q_{\max} = C_1 U_{\max} = 1^{-3} \text{ C}$$

$$U_1 = U_{\max} = 100 \text{ V}, U_2 = Q_{\max}/C_2 = 50 \text{ V}, U_3 = Q_{\max}/C_3 = 40 \text{ V}$$


$$\Rightarrow U = U_1 + U_2 + U_3 = 190 \text{ V}$$

$$(b) \Rightarrow E = \frac{1}{2}C_1 U_1^2 + \frac{1}{2}C_2 U_2^2 + \frac{1}{2}C_3 U_3^2 = 9.5 \times 10^{-2} \text{ J}$$

2

A parallel-plate capacitor of plate area $A = 10.5\text{cm}^2$ and plate separation $2d = 7.12 \text{ mm}$. The left half of the gap is filled with material of dielectric constant $\kappa_1 = 21.0$; the top of the right half is filled with material of dielectric constant $\kappa_2 = 42.0$; the bottom of the right half is filled with material of dielectric constant $\kappa_3 = 58.0$. What is the capacitance?

Reference:

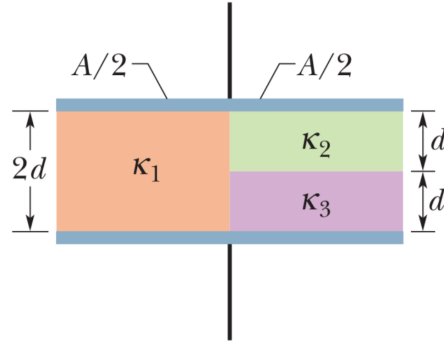

$$\Rightarrow C_1 = \frac{\epsilon_0 \kappa_1 A/2}{2d}, C_2 = \frac{\epsilon_0 \kappa_2 A/2}{d}, \frac{\epsilon_0 \kappa_3 A/2}{d}$$

$$\Rightarrow C = C_1 + \frac{1}{\frac{1}{C_2} + \frac{1}{C_3}} = \frac{\epsilon_0 A}{2d} \left(\frac{\kappa_1}{2} + \frac{1}{\frac{1}{\kappa_2} + \frac{1}{\kappa_3}} \right) = 4.55 \times 10^{-11} \text{ F}$$

3

The rain-soaked shoes of a person may explode if ground current from nearby vaporizes the water. The sudden conversion of water to water vapor causes a dramatic expansion that can rip apart shoes. Water has density 1000 kg / m³ and requires 2256 kJ / kg to be vaporized. If horizontal current lasts 2.00 ms and encounters water with resistivity 150Ω·m, length 12.0cm, and vertical cross-sectional area 15 × 10⁻⁵ m², what average current is required to vaporize the water?

Reference:


$$\Rightarrow R = \rho_R \frac{l}{A} \text{ and } E = Lm\rho Al$$

$$\text{and from } \bar{I}^2 R t = E \text{ we can get that } \bar{I} = \sqrt{\frac{E}{tR}} = 13.0$$

4

There is a rod of resistive material (Figure a). The resistance per unit length of the rod increases in the positive direction of the x axis. At any position x along the rod, the resistance dR of a narrow (differential) section of width dx is given by $dR = 5.00dx$ where dR is in ohms and x is in meters. Figure b shows such a narrow section. You are to slice off a length of the rod between $x = 0$ and some position $x = L$ and then connect that length to a battery with potential difference $V = 5.0 \text{ V}$ (Figure c). You want the current in the length to transfer energy to thermal energy at the rate of 200 W. At what position $x = L$ should you cut the rod?

Reference:

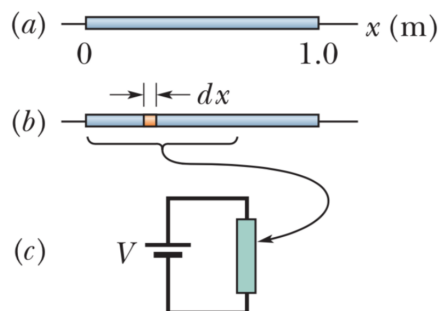


$$\Rightarrow R = \int_0^L 5.00x dx = 2.50L^2 = \frac{U^2}{P} \Rightarrow L = 0.224 \text{ m}$$

5

In a circuit, $\varepsilon = 1.2 \text{ kV}$, $C = 6.5 \mu\text{F}$, $R_1 = R_2 = R_3 = 0.73 \text{ M}\Omega$. With C completely uncharged, switch S is suddenly closed (at $t = 0$).

At $t = 0$, what are (a) current i_1 in resistor 1, (b) current i_2 in resistor 2, and (c) current i_3 in resistor 3?

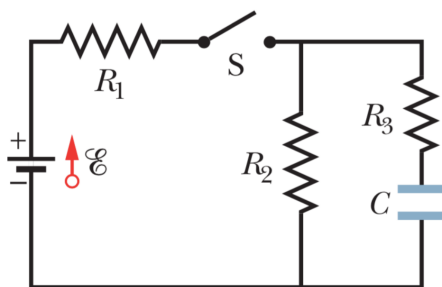At $t = \infty$ (that is, after many time constants), what are (d) i_1 , (e) i_2 , and (f) i_3 ? What is the potential difference V_2 across resistor 2 at (g) $t = 0$ and (h) $t = \infty$ (i) Sketch V_2 versus t between these two extreme times.



Reference:

$$(a) R = R_1 + \frac{R_2 R_3}{R_2 + R_3} \Rightarrow i_1 = \frac{\varepsilon}{R} = 1.10 \text{ mA}$$

$$(b)(c) \Rightarrow i_2 = i_3 = \frac{1}{2} i_1 = 0.548 \text{ mA}$$


$$(d)(e) \Rightarrow i_1 = i_2 = \frac{\varepsilon}{R_1 + R_2} = 0.822 \text{ mA}$$

$$(f) \Rightarrow i_3 = 0$$

$$(g) \Rightarrow V_2 = \frac{R - R_2}{R} \varepsilon = 0.4 \text{ kV}$$


$$(h) \Rightarrow v_2 = \frac{R_2}{R_1 + R_2} \varepsilon = 0.6 \text{ kV}$$

(i)

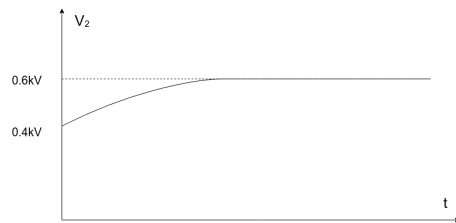


6

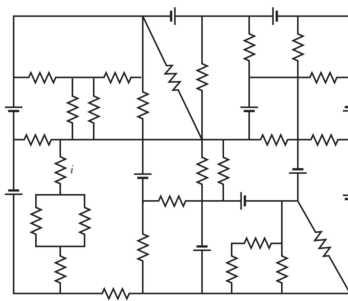What are the (a) size and (b) direction (up or down) of current i , where all resistances are 4.0Ω and all batteries are ideal and have an emf of 10 V ? (Hint: Find a special loop such that you can answer by mental calculation only.)



Reference:

(a)(b) consider the circuit shown below:

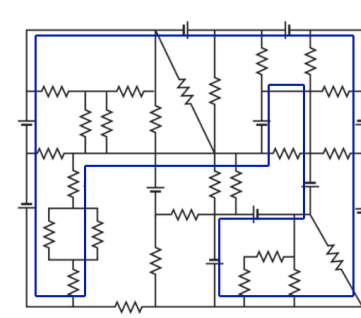

$$\Rightarrow i = \frac{(7-3)\varepsilon}{R+R+\frac{R^2}{R+R}} = 4.0\text{ A, the direction is up}$$

7

A metal sphere of radius 15 cm has a net charge of 3.0×10^{-8} C.


- What is the electric field at the sphere's surface?
- If $V = 0$ at infinity, what is the electric potential at the sphere's surface?
- At what distance from the sphere's surface has the electric potential decreased by 500 V?

Reference:

- $\Rightarrow E = \frac{q}{4\pi\epsilon_0 r^2} = 1.20 \times 10^4$ V/m, perpendicular to the surface
- $\Rightarrow V = \frac{q}{4\pi\epsilon_0 r} = 1.80 \times 10^3$ V
- $\Rightarrow \Delta V = \frac{q}{4\pi\epsilon_0 r} - \frac{q}{4\pi\epsilon_0 (r+d)} \Rightarrow d = 5.78$ cm

8

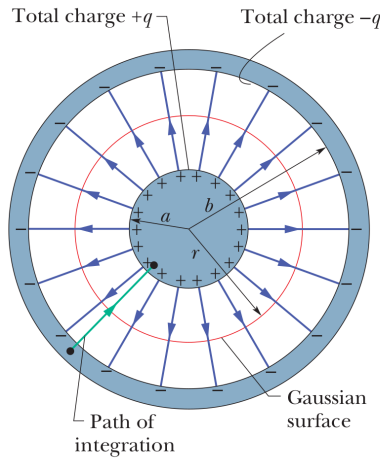Consider two concentric spherical shells, of radii a and b . Show that the capacitance of the shells is $C = 4\pi\epsilon_0 \frac{ab}{b-a}$. What is the capacitance to a single isolated spherical conductor of radius R , then?



Reference:

$$\begin{aligned} \Rightarrow \Delta U &= \frac{Q}{4\pi\epsilon_0 a} - \frac{Q}{4\pi\epsilon_0 b} = \frac{Q}{4\pi\epsilon_0} \cdot \frac{b-a}{ab} \\ \Rightarrow C &= \frac{Q}{\Delta U} = \frac{4\pi\epsilon_0 (b-a)}{ab} \end{aligned}$$

9

Show that the curl of a central force $\vec{F}(\vec{r}) = f(r)\hat{r}$ is zero, i.e. $\nabla \times \vec{F}(\vec{r}) = \vec{0}$. Hence, central forces are conservative.

Reference:

$$\Rightarrow \int \vec{F}(\vec{r}) \cdot d\vec{s} = \int f(r) \hat{r} \cdot (d\vec{r} + dr_{\theta} \vec{e}_{\theta} + dr_{\phi} \vec{e}_{\phi}) = \int f(r) dr$$

that is, the work done by the force is independent of the path, so the force is conservative, $\nabla \times \vec{F}(\vec{r}) = \vec{0}$

10

Consider a two-dimensional electric field $\vec{E}(x, y) = \frac{-y\hat{i} + x\hat{j}}{x^2 + y^2}$.

(a) Calculate the curl of the field $\nabla \times \vec{E}$.

(b) Show that the circulation of the field $\Gamma = \oint_C \vec{E} \cdot d\vec{s} = 2\pi$ around a unit circle centered at origin. Therefore, a vanishing curl does not implies, in general, that the force is conservative. They are equivalent only when the space is simply connected.

Reference:

$$(a) \Rightarrow \nabla \times \vec{E}(x, y) = \left(\frac{\partial}{\partial x}, \frac{\partial}{\partial y}\right) \times \left(\frac{-y}{x^2 + y^2}, \frac{x}{x^2 + y^2}\right) = \left(\frac{y^2 - x^2}{x^2 + y^2} + \frac{x^2 - y^2}{x^2 + y^2}\right) \vec{k} = \vec{0}$$

(b) let $x = \cos \theta, y = \sin \theta$

$$\Rightarrow \vec{E}(x, y) = -\sin \theta \vec{i} + \cos \theta \vec{j} \text{ and } d\vec{s} = d(\cos \theta \vec{i} + \sin \theta \vec{j}) = (-\sin \theta \vec{i} + \cos \theta \vec{j}) d\theta$$

$$\Rightarrow \Gamma = \oint_C \vec{E} \cdot d\vec{s} = \int_0^{2\pi} (\sin^2 \theta + \cos^2 \theta) d\theta = 2\pi$$